



# Resonant-Free PDN Design<sup>®</sup>

Mart Coenen, EMCMCC, Eindhoven, the Netherlands  
Arthur van Roermund, Eindhoven University of Technology  
Mixed-signal Microelectronics, Eindhoven, the Netherlands  
[mart.coenen@emcmcc.nl](mailto:mart.coenen@emcmcc.nl), [a.h.m.v.roermund@tue.nl](mailto:a.h.m.v.roermund@tue.nl)



## Resonant Free PDN Design

### Presentation outline

- Introduction
- Overview
- New approach
- Conclusions



## Introduction

- With nanometre scaling, the amount of transistors/chip will follow Moore's Law.
- On- and off-chip clock and data speeds will increase further.
- Core supply voltages are reduced further down to below 1 Volt
- Peripheral supply voltages have to follow international agreed voltages levels to enable interfacing.



## Introduction

- While lowering the core supply voltages, the on-chip noise margin will drop accordingly
- Tight on- and off-chip decoupling measures are necessary.
- Typically, RF switching noise from digital designs are forced out of their packages through the supply and ground pins when applying conventional off-chip decoupling




### Overview of measures

- On-chip measures
  - On-chip decoupling; needed for operation
  - Spread-spectrum; spreading in frequency domain
  - Multi-phase clocking; spreading in time domain
  - Embedded LDO; current confinement
  - Variable voltage, variable frequency
- Off-chip measures
  - Kelvin contacts
  - Complementary off-chip measures
  - Resonance free PDN design




### Overview (of what has been done)

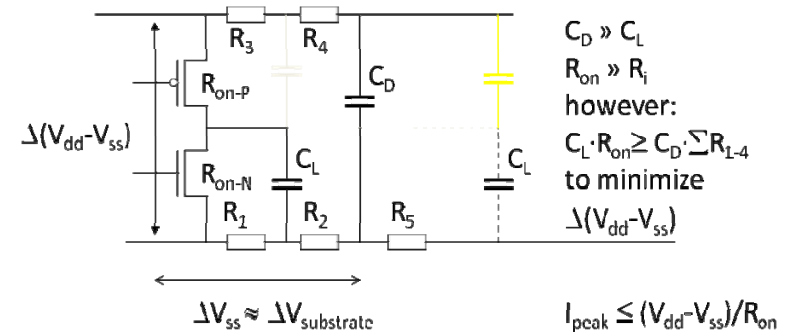

- Supply bounce; IR-drop and delay
- $V_{ss}$ -net/substrate analysis



### Overview (of what has been done)

 

Current confinement by Kelvin contacts for Off-chip decoupling



### New approach

- On-chip decoupling is always present:  $\mu C$ , DSP, FPGA, etc. both for core and peripherals
- Equivalent package induction with on-chip capacitance is at resonance below 100 MHz: example: 200 nF + 0,2 nH  $\rightarrow$  ~25 MHz
- When ideally decoupled off-chip quality factor of resonance > 10 is reached
- Need for dampening !! (in example just 31 m $\Omega$  !!)




## New approach

- Multiple decoupling capacitors are root cause for resonances. Values: 1:10:100:1000 are typ. placed in parallel to cover whole frequency range. ESL and physical distance add inductances thus resonances
- Multiple supply/ground planes in parallel in a multilayer PCB structure are additional root cause for resonances. Open and short-circuited TL-ends cause steep resonances from several MHz into GHz range



 
## New approach

- Ceramic multilayer capacitors have resonance frequency in GHz range with  $Q > 1000$ , larger capacitance  $\rightarrow$  lower ESR



## Multiple decaps in parallel

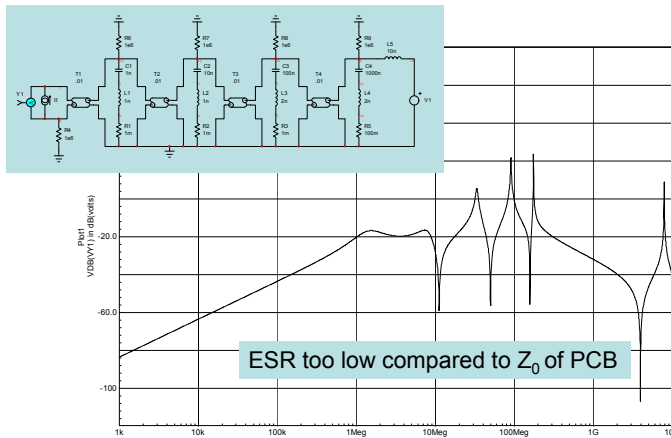


## New approach

- Inter-plane characteristic impedance is between 0,1 and 2,5  $\Omega$ . Multiple plane pairs can be used in parallel
- Port impedance is  $Z_0/4$  as signals are propagation to all 4 edges or when rotation symmetric diverging;  $Z_0/2\pi$
- Port impedances less than 10 m $\Omega$  easy achievable; 3 plane pairs at 100  $\mu$ m spacing


 
### Off-center port on Euro-card, $Z_0 = 10 \text{ m}\Omega$




### New approach


- The whole PDN chain from DC supply to the IC supply pads needs to be considered
- All “taps” and “feeds” shall:
  - impedance  $\gg Z_0/4 \geq f_{crit}$ .
  - resonant free;  $Q \leq 2$
- Due to skin and proximity effects full insulation between supply/ground currents and signal return paths are achieved  
skin depth =  $6 \mu\text{m}$  @ 100 MHz, Cu-layer =  $37 \mu\text{m}$




### Total Resonant-Free PDN solution

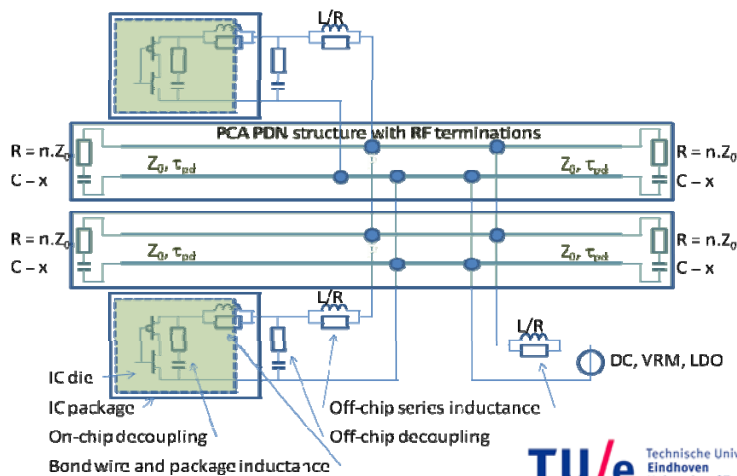


### Device port impedance $Z_{11}$

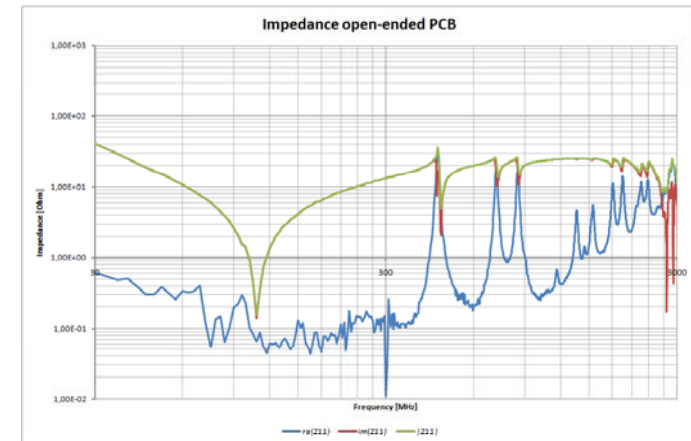


 

## Device port impedance $Z_{11}$

 

## Device port impedance $Z_{11}$

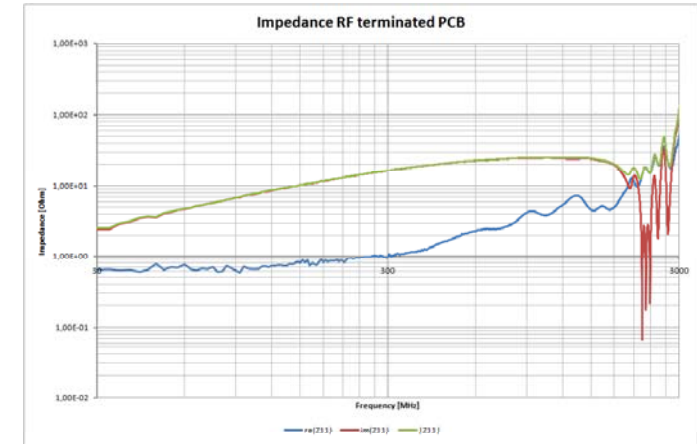

## Conclusions

- Each part of the PDN chain shall be optimally dampened, by using: series inductance + series resistance or Kelvin contacts
- Decoupling capacitors shall be optimised for ESR too, ESL remains less critical
- Off-chip decoupling, through short PDNs, is too late for decoupling in the sub-ns region (due to self-resonance (skew) and delay of the device's PDN and in its package)
- Resonant-Free PDN is an option.